

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

1. In a series circuit if $V = 100\angle -30^\circ$ volt and $I = 10\angle -10^\circ$ A. What is the nature of circuit?
 - i) Resistive
 - ii) Capacitive
 - iii) Inductive
 - iv) Resonating
2. In a series RLC circuit what is the angle between voltage across L and voltage across C in a phasor diagram?
 - i) 0°
 - ii) 180°
 - iii) 90°
 - iv) 45°
3. Which of the following is **not** a condition for series resonance?
 - i) $Z=R$
 - ii) $\cos \Phi=0$
 - iii) $X_L=X_C$
 - iv) $\Phi=0^\circ$
4. Which of the following is incorrect for balanced three phase star load?
 - i) $I_{ph} = I_L$
 - ii) $V_{ph} < V_L$
 - iii) $Z_{ph} = V_{ph}/I_{ph}$
 - iv) $V_{ph} > V_L$
5. Which of the following is **not** the formula for the average power in a single phase resistive AC circuit?
 - i) $V_m I_m \cos \Phi$
 - ii) $I_{rms}^2 R$
 - iii) $0.5 V_m I_m$
 - iv) $V_{rms} I_{rms}$
6. Which of the following is incorrect for balanced three phase delta load?
 - i) $I_{ph} = I_L$
 - ii) $V_{ph} = V_L$
 - iii) $Z_{ph} = V_{ph}/I_{ph}$
 - iv) $I_L > I_{ph}$
7. What is the instantaneous value of $v(t)=10 \sin (314t+30^\circ)$, for $t = 1\text{sec}$?
 - i) 0
 - ii) 3.56V
 - iii) 5V
 - iv) -2.7V
8. Which of the following is incorrect phase sequence?
 - (i) R – Y – B
 - (ii) B – R – Y
 - (iii) Y – B – R
 - (iv) B – Y – R
9. $v(t) = 10 \sin (314t+10^\circ)$ and $i(t) = 5 \sin (314t-45^\circ)$. The power factor is
 - (i) 0.2588
 - (ii) 0.866
 - (iii) 0.707
 - (iv) 0.5736
10. Which of the following is incorrect statement?
 - (i) $Z_{ph} = V_{ph}/I_{ph}$ for star or delta load
 - (ii) $Z_{ph} = V_L/I_{ph}$ for delta load
 - (iii) $Z_{ph} = V_{ph}/I_L$ for delta load
 - (iv) $Z_{ph} = V_{ph}/I_L$ for star load

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

11. Three phase 440V, 50Hz is supplied to balanced delta load consisting of phase impedance $Z = 6+j8 \Omega$. The phase current will be ____.
- (i) 44A
 - (ii) 22A
 - (iii) 11A
 - (iv) $44/\sqrt{3}$ A
12. Which of the following is a **correct** statement, in case of sinusoidal waveform ?
- (i) Form Factor = 0.707
 - (ii) Form Factor = 0.637
 - (iii) Form Factor = 1.414
 - (iv) Form Factor = 1.11
13. Which one of the following is **not** correct?
- (i) $V_{ph} = V_L$ for delta
 - (ii) $V_{ph} = V_L/\sqrt{3}$ for star
 - (iii) $I_{ph} = V_{ph}/Z_{ph}$
 - (iv) $I_L = I_{ph}$ for delta
14. Three phase 440V, 50Hz is supplied to balanced star load consisting of phase impedance $Z = 6+j8 \Omega$. The phase current will be ____.
- (i) 44A
 - (ii) 22A
 - (iii) 11A
 - (iv) $44/\sqrt{3}$ A
15. Which one of the following is **not** quality factor formula for series resonance?
- (i) $\frac{1}{R} \sqrt{\frac{L}{C}}$
 - (ii) $\frac{\text{Voltage across Capacitor}}{\text{Supply Voltage}}$
 - (iii) $\frac{\text{Voltage across Inductor}}{\text{Supply Voltage}}$
 - (iv) $\frac{\text{Voltage across Resistor}}{\text{Supply Voltage}}$
16. In case of parallel resonance the current flowing through the circuit is
- (i) Minimum
 - (ii) Zero
 - (iii) Maximum
 - (iv) Infinite
17. Three phase 440V, 50Hz is supplied to balanced delta load consisting of phase impedance $Z = 6+j8 \Omega$. The line current will be ____.
- (i) 44A
 - (ii) 22A
 - (iii) $44\sqrt{3}$ A
 - (iv) $44/\sqrt{3}$ A
18. Three phase 440V, 50Hz is supplied to balanced star load consisting of phase impedance $Z = 6+j8 \Omega$. The line current will be ____.
- (i) 44A
 - (ii) 22A
 - (iii) 11A
 - (iv) $44/\sqrt{3}$ A
19. Current leads voltage by 90° for which type of element?
- (i) purely resistive
 - (ii) purely inductive
 - (iii) purely capacitive
 - (iv) series R-L

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

20. What is the phase angle of three phase balanced star connected load impedance if $V_L = 100\angle 90^\circ$ V and $I_L = 10\angle 20^\circ$ A?
(i) 60°
(ii) 40°
(iii) 30°
(iv) 70°
21. Voltage leads current by 90° for which type of element?
(i) purely resistive
(ii) purely inductive
(iii) purely capacitive
(iv) series R-C
22. What is the value of three phase balanced star connected load impedance if $V_L = 100\angle 90^\circ$ V and $I_L = 10\angle 20^\circ$ A?
(i) 10Ω
(ii) $10/\sqrt{3}\Omega$
(iii) $10\sqrt{3}\Omega$
(iv) 100Ω
23. What is the phase angle of three phase balanced delta connected load impedance if $V_{ph} = 100\angle 100^\circ$ V and $I_L = 10\angle 20^\circ$ A?
(i) 120°
(ii) 80°
(iii) 30°
(iv) 50°
24. The dynamic impedance in case of parallel resonance is given by _____.
(i) RC/L
(ii) L/RC
(iii) LR/C
(iv) LC/R
25. What is the value of three phase balanced delta connected load impedance if $V_L = 100\angle 100^\circ$ V and $I_L = 10\angle 20^\circ$ A?
(i) 10Ω
(ii) $10/\sqrt{3}\Omega$
(iii) $10\sqrt{3}\Omega$
(iv) 100Ω
26. To represent phasors in the same phasor diagram _____ has to be same.
(i) frequency
(ii) phase
(iii) amplitude
(iv) rms values
27. Which of the following is incorrect statement for power factor in series circuit?
(i) $\text{pf} = \cos\phi$
(ii) $\text{pf} = \text{Voltage across R/Supply voltage}$
(iii) $\text{pf} = R/Z$
(iv) $\text{pf} = S/P$
28. The phase difference between inductor current and capacitor current for parallel resonance circuit is _____.
(i) 90°
(ii) more than 90°
(iii) less than 90°
(iv) 0°

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

29. What is the value of impedance of the series circuit if power loss is 200W with current as 10A. The power factor is 0.8 lagging?
- i) 2Ω
 - ii) 2.5Ω
 - iii) 5Ω
 - iv) 10Ω
30. What is the nature of three phase balanced delta connected load impedance if $V_{ph} = 100\angle -50^\circ$ V and $I_L = 10\angle -80^\circ$ A?
- (i) Inductive
 - (ii) Resistive
 - (iii) Capacitive
 - (iv) Purely Inductive
31. In parallel AC circuits the admittances get _____.
- i) added
 - ii) multiplied
 - iii) subtracted
 - iv) remains same
32. The values of conductance and susceptance (in mho) for $Z = 8 + j6\Omega$ respectively are _____.
- i) 0.8, 0.1
 - ii) 0.6, 0.8
 - iii) 0.8, 0.5
 - iv) 0.8, 0.6
- 0.08, -0.06*
33. The quality factor in series resonance is _____.
- i) Current magnification
 - ii) Voltage magnification
 - iii) always equal to 1
 - iv) less than 1
34. If series RLC circuit is inductive in nature ($X_L > X_C$). What is the angle between voltage across capacitor and supply voltage?
- i) 90°
 - ii) $90^\circ - \phi$
 - iii) $90^\circ + \phi$
 - iv) $30^\circ - \phi$
35. If series RLC circuit is inductive in nature ($X_L > X_C$). What is the angle between voltage across inductor and supply voltage?
- i) 90°
 - ii) $90^\circ - \phi$
 - iii) $90^\circ + \phi$
 - iv) $30^\circ - \phi$
36. If series RLC circuit is capacitive in nature ($X_L < X_C$). What is the angle between voltage across capacitor and supply voltage?
- i) 90°
 - ii) $90^\circ - \phi$
 - iii) $90^\circ + \phi$
 - iv) $30^\circ - \phi$

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

37. If series RLC circuit is capacitive in nature ($X_L < X_C$). What is the angle between voltage across inductor and supply voltage?
- i) 90°
 - ii) $90^\circ - \phi$
 - iii) $90^\circ + \phi$
 - iv) $30^\circ - \phi$
38. For series RLC circuit $\phi = 0^\circ$, the supply voltage is 100V. what is the value of quality factor if voltage across inductor is 500V?
- i) 2
 - ii) 1
 - iii) 5
 - iv) 3
39. The quality factor in parallel resonance is _____.
- i) Current magnification
 - ii) Voltage magnification
 - iii) always equal to 1
 - iv) always less than 1
40. What is the nature of three phase balanced star connected load impedance if $V_{ph} = 100\angle -50^\circ$ V and $I_L = 10\angle -60^\circ$ A?
- (i) Inductive
 - (ii) Resistive
 - (iii) Capacitive
 - (iv) Purely Inductive
41. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of impedance?
- i) 60.7266Ω
 - ii) 5.905Ω
 - iii) 63.858Ω
 - iv) 60.5204Ω
42. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of current?
- i) 38.9497
 - ii) 3.7875A
 - iii) 3.6017A
 - iv) 4A
43. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of phase angle?
- i) 32.14
 - ii) 45°
 - iii) 85.28°
 - iv) 90°
- -85.28°
44. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of active power?
- i) 100W
 - ii) 68.1653W
 - iii) 7.5855kW
 - iv) 71.6817W

Vidyalankar Institute of Technology
Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank

45. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of reactive power?
i) 868.1708VAR
ii) 4.7658kVAR
iii) 825.5817VAR
iv) 100VAR
46. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of apparent power?
i) 828.391VA
ii) 871.125VA
iii) 8.9584kVA
iv) 1kVA
47. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the value of power factor?
i) 0.0823 (Lagging)
ii) 0.823 (Leading)
iii) 0.0823 (Leading)
iv) unity
48. A series R-L-C circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ and $C = 50\mu\text{F}$ connected to single phase ac 230V,50Hz supply. What is the nature of circuit?
i) Resistive
ii) Resonating
iii) Capacitive
iv) Inductive
49. A series R-L circuit consists of $R = 5\Omega$, $L = 10\text{mH}$ connected to single phase ac 230V,50Hz supply. What is the value of capacitor to be connected in parallel with RL circuit to achieve resonance?
i) 286.782 μF
ii) 286.782pF
iii) 286.782mF
iv) 286.782F
50. A series R-L circuit consists of $R = 5\Omega$, $L = 10\text{mH}$. and $C = 50\mu\text{F}$ connected to single phase ac 230V supply. What is the value of resonant frequency?
i) 50Hz
ii) 314Hz
iii) 225.08Hz
iv) 500Hz