

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

1. In a series circuit if  $V = 100\angle -30^\circ$  volt and  $I = 10\angle -10^\circ$  A. What is the nature of circuit?
  - i) Resistive
  - ii) Capacitive
  - iii) Inductive
  - iv) Resonating
2. In a series RLC circuit what is the angle between voltage across L and voltage across C in a phasor diagram?
  - i)  $0^\circ$
  - ii)  $180^\circ$
  - iii)  $90^\circ$
  - iv)  $45^\circ$
3. Which of the following is **not** a condition for series resonance?
  - i)  $Z=R$
  - ii)  $\cos \Phi=0$
  - iii)  $X_L=X_C$
  - iv)  $\Phi=0^\circ$
4. Which of the following is incorrect for balanced three phase star load?
  - i)  $I_{ph} = I_L$
  - ii)  $V_{ph} < V_L$
  - iii)  $Z_{ph} = V_{ph}/I_{ph}$
  - iv)  $V_{ph} > V_L$
5. Which of the following is **not** the formula for the average power in a single phase resistive AC circuit?
  - i)  $V_m I_m \cos \Phi$
  - ii)  $I_{rms}^2 R$
  - iii)  $0.5 V_m I_m$
  - iv)  $V_{rms} I_{rms}$
6. Which of the following is incorrect for balanced three phase delta load?
  - i)  $I_{ph} = I_L$
  - ii)  $V_{ph} = V_L$
  - iii)  $Z_{ph} = V_{ph}/I_{ph}$
  - iv)  $I_L > I_{ph}$
7. What is the instantaneous value of  $v(t)=10 \sin (314t+30^\circ)$ , for  $t = 1\text{sec}$ ?
  - i) 0
  - ii) 3.56V
  - iii) 5V
  - iv) -2.7V
8. Which of the following is incorrect phase sequence?
  - (i) R – Y – B
  - (ii) B – R – Y
  - (iii) Y – B – R
  - (iv) B – Y – R
9.  $v(t) = 10 \sin (314t+10^\circ)$  and  $i(t) = 5 \sin (314t-45^\circ)$ . The power factor is
  - (i) 0.2588
  - (ii) 0.866
  - (iii) 0.707
  - (iv) 0.5736
10. Which of the following is incorrect statement?
  - (i)  $Z_{ph} = V_{ph}/I_{ph}$  for star or delta load
  - (ii)  $Z_{ph} = V_L/I_{ph}$  for delta load
  - (iii)  $Z_{ph} = V_{ph}/I_L$  for delta load
  - (iv)  $Z_{ph} = V_{ph}/I_L$  for star load

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

11. Three phase 440V, 50Hz is supplied to balanced delta load consisting of phase impedance  $Z = 6+j8 \Omega$ . The phase current will be \_\_\_\_.
- (i) 44A
  - (ii) 22A
  - (iii) 11A
  - (iv)  $44/\sqrt{3}$  A
12. Which of the following is a **correct** statement, in case of sinusoidal waveform ?
- (i) Form Factor = 0.707
  - (ii) Form Factor = 0.637
  - (iii) Form Factor = 1.414
  - (iv) Form Factor = 1.11
13. Which one of the following is **not** correct?
- (i)  $V_{ph} = V_L$  for delta
  - (ii)  $V_{ph} = V_L/\sqrt{3}$  for star
  - (iii)  $I_{ph} = V_{ph}/Z_{ph}$
  - (iv)  $I_L = I_{ph}$  for delta
14. Three phase 440V, 50Hz is supplied to balanced star load consisting of phase impedance  $Z = 6+j8 \Omega$ . The phase current will be \_\_\_\_.
- (i) 44A
  - (ii) 22A
  - (iii) 11A
  - (iv)  $44/\sqrt{3}$  A
15. Which one of the following is **not** quality factor formula for series resonance?
- (i)  $\frac{1}{R} \sqrt{\frac{L}{C}}$
  - (ii)  $\frac{\text{Voltage across Capacitor}}{\text{Supply Voltage}}$
  - (iii)  $\frac{\text{Voltage across Inductor}}{\text{Supply Voltage}}$
  - (iv)  $\frac{\text{Voltage across Resistor}}{\text{Supply Voltage}}$
16. In case of parallel resonance the current flowing through the circuit is
- (i) Minimum
  - (ii) Zero
  - (iii) Maximum
  - (iv) Infinite
17. Three phase 440V, 50Hz is supplied to balanced delta load consisting of phase impedance  $Z = 6+j8 \Omega$ . The line current will be \_\_\_\_.
- (i) 44A
  - (ii) 22A
  - (iii)  $44\sqrt{3}$  A
  - (iv)  $44/\sqrt{3}$  A
18. Three phase 440V, 50Hz is supplied to balanced star load consisting of phase impedance  $Z = 6+j8 \Omega$ . The line current will be \_\_\_\_.
- (i) 44A
  - (ii) 22A
  - (iii) 11A
  - (iv)  $44/\sqrt{3}$  A
19. Current leads voltage by  $90^\circ$  for which type of element?
- (i) purely resistive
  - (ii) purely inductive
  - (iii) purely capacitive
  - (iv) series R-L

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

20. What is the phase angle of three phase balanced star connected load impedance if  $V_L = 100\angle 90^\circ$  V and  $I_L = 10\angle 20^\circ$  A?  
(i)  $60^\circ$   
(ii)  $40^\circ$   
(iii)  $30^\circ$   
(iv)  $70^\circ$
21. Voltage leads current by  $90^\circ$  for which type of element?  
(i) purely resistive  
(ii) purely inductive  
(iii) purely capacitive  
(iv) series R-C
22. What is the value of three phase balanced star connected load impedance if  $V_L = 100\angle 90^\circ$  V and  $I_L = 10\angle 20^\circ$  A?  
(i)  $10\Omega$   
(ii)  $10/\sqrt{3}\Omega$   
(iii)  $10\sqrt{3}\Omega$   
(iv)  $100\Omega$
23. What is the phase angle of three phase balanced delta connected load impedance if  $V_{ph} = 100\angle 100^\circ$  V and  $I_L = 10\angle 20^\circ$  A?  
(i)  $120^\circ$   
(ii)  $80^\circ$   
(iii)  $30^\circ$   
(iv)  $50^\circ$
24. The dynamic impedance in case of parallel resonance is given by \_\_\_\_\_.  
(i)  $RC/L$   
(ii)  $L/RC$   
(iii)  $LR/C$   
(iv)  $LC/R$
25. What is the value of three phase balanced delta connected load impedance if  $V_L = 100\angle 100^\circ$  V and  $I_L = 10\angle 20^\circ$  A?  
(i)  $10\Omega$   
(ii)  $10/\sqrt{3}\Omega$   
(iii)  $10\sqrt{3}\Omega$   
(iv)  $100\Omega$
26. To represent phasors in the same phasor diagram \_\_\_\_\_ has to be same.  
(i) frequency  
(ii) phase  
(iii) amplitude  
(iv) rms values
27. Which of the following is incorrect statement for power factor in series circuit?  
(i)  $\text{pf} = \cos\phi$   
(ii)  $\text{pf} = \text{Voltage across R} / \text{Supply voltage}$   
(iii)  $\text{pf} = R/Z$   
(iv)  $\text{pf} = S/P$  P/S
28. The phase difference between inductor current and capacitor current for parallel resonance circuit is \_\_\_\_\_.  
(i)  $90^\circ$   
(ii) more than  $90^\circ$   
(iii) less than  $90^\circ$   
(iv)  $0^\circ$

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

29. What is the value of impedance of the series circuit if power loss is 200W with current as 10A. The power factor is 0.8 lagging?
- i)  $2\Omega$
  - ii)  $2.5\Omega$
  - iii)  $5\Omega$
  - iv)  $10\Omega$
30. What is the nature of three phase balanced delta connected load impedance if  $V_{ph} = 100\angle -50^\circ$  V and  $I_L = 10\angle -80^\circ$  A?
- (i) Inductive
  - (ii) Resistive
  - (iii) Capacitive
  - (iv) Purely Inductive
31. In parallel AC circuits the admittances get \_\_\_\_\_.
- i) added
  - ii) multiplied
  - iii) subtracted
  - iv) remains same
32. The values of conductance and susceptance (in mho ) for  $Z = 8 + j6\Omega$  respectively are \_\_\_\_\_.
- i) 0.8, 0.1
  - ii) 0.6, 0.8
  - iii) 0.8, 0.5
  - iv) 0.8, 0.6
33. The quality factor in series resonance is \_\_\_\_\_.
- i) Current magnification
  - ii) Voltage magnification
  - iii) always equal to 1
  - iv) less than 1
34. If series RLC circuit is inductive in nature ( $X_L > X_C$ ). What is the angle between voltage across capacitor and supply voltage?
- i)  $90^\circ$
  - ii)  $90^\circ - \phi$
  - iii)  $90^\circ + \phi$
  - iv)  $30^\circ - \phi$
35. If series RLC circuit is inductive in nature ( $X_L > X_C$ ). What is the angle between voltage across inductor and supply voltage?
- i)  $90^\circ$
  - ii)  $90^\circ - \phi$
  - iii)  $90^\circ + \phi$
  - iv)  $30^\circ - \phi$
36. If series RLC circuit is capacitive in nature ( $X_L < X_C$ ). What is the angle between voltage across capacitor and supply voltage?
- i)  $90^\circ$
  - ii)  $90^\circ - \phi$
  - iii)  $90^\circ + \phi$
  - iv)  $30^\circ - \phi$

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

37. If series RLC circuit is capacitive in nature ( $X_L < X_C$ ). What is the angle between voltage across inductor and supply voltage?  
i)  $90^\circ$   
ii)  $90^\circ - \phi$   
iii)  $90^\circ + \phi$   
iv)  $30^\circ - \phi$
38. For series RLC circuit  $\phi = 0^\circ$ , the supply voltage is 100V. what is the value of quality factor if voltage across inductor is 500V?  
i) 2  
ii) 1  
iii) 5  
iv) 3
39. The quality factor in parallel resonance is \_\_\_\_\_.  
i) Current magnification  
ii) Voltage magnification  
iii) always equal to 1  
iv) always less than 1
40. What is the nature of three phase balanced star connected load impedance if  $V_{ph} = 100\angle -50^\circ$  V and  $I_L = 10\angle -60^\circ$  A?  
(i) Inductive  
(ii) Resistive  
(iii) Capacitive  
(iv) Purely Inductive
41. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of impedance?  
i)  $60.7266\Omega$   
ii)  $5.905\Omega$   
iii)  $63.858\Omega$   
iv)  $60.5204\Omega$
42. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of current?  
i) 38.9497  
ii) 3.7875A  
iii) 3.6017A  
iv) 4A
43. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of phase angle?  
i) 32.14  
ii)  $45^\circ$   
iii)  $85.28^\circ$   
iv)  $90^\circ$
44. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of active power?  
i) 100W  
ii) 68.1653W  
iii) 7.5855kW  
iv) 71.6817W

**Vidyalankar Institute of Technology**  
**Sem 1 (All courses) IA-2 – Basic Electrical Engineering Question Bank**

45. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of reactive power?
- i) 868.1708VAR
  - ii) 4.7658kVAR
  - iii) 825.5817VAR
  - iv) 100VAR
46. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of apparent power?
- i) 828.391VA
  - ii) 871.125VA
  - iii) 8.9584kVA
  - iv) 1kVA
47. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the value of power factor?
- i) 0.0823 (Lagging)
  - ii) 0.823 (Leading)
  - iii) 0.0823 (Leading)
  - iv) unity
48. A series R-L-C circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  and  $C = 50\mu\text{F}$  connected to single phase ac 230V,50Hz supply. What is the nature of circuit?
- i) Resistive
  - ii) Resonating
  - iii) Capacitive
  - iv) Inductive
49. A series R-L circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$  connected to single phase ac 230V,50Hz supply. What is the value of capacitor to be connected in parallel with RL circuit to achieve resonance?
- i)  $286.782\mu\text{F}$
  - ii)  $286.782\text{pF}$
  - iii)  $286.782\text{mF}$
  - iv)  $286.782\text{F}$
50. A series R-L circuit consists of  $R = 5\Omega$ ,  $L = 10\text{mH}$ . and  $C = 50\mu\text{F}$  connected to single phase ac 230V supply. What is the value of resonant frequency?
- i) 50Hz
  - ii) 314Hz
  - iii) 225.08Hz
  - iv) 500Hz